

# Inductance

FIZ102E: Electricity & Magnetism



Yavuz Ekşi

İTÜ, Fizik Müh. Böl.

# Contents

- 1 Mutual inductance
- 2 Self-inductance and inductors
- 3 Magnetic field energy
- 4 R-L circuit


## Learning outcomes

- How a time-varying current in one coil can induce an emf in a second, unconnected coil.
- How to relate the induced emf in a circuit to the rate of change of current in the same circuit.
- How to calculate the energy stored in a magnetic field.
- How to analyze circuits that include both a resistor and an inductor (coil).
- Why electrical oscillations occur in circuits that include both an inductor and a capacitor.
- Why oscillations decay in circuits with an inductor, a resistor, and a capacitor.

# Introduction

- A changing current in a coil induces an emf in an adjacent coil. The coupling between the coils is described by their *mutual inductance*.
- A changing current in a coil also induces an emf in that same coil.
- Such a coil is called an *inductor*,
- and the relationship of current to emf is described by the inductance (also called *self-inductance*) of the coil.

# Mutual inductance

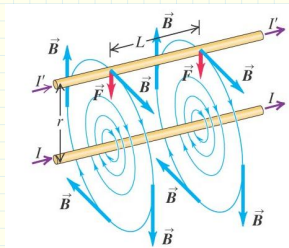


Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley.

- We have considered the magnetic interaction between two wires carrying steady currents.
- The current in one wire causes a magnetic field, which exerts a force on the current in the second wire.
- An additional interaction arises between two circuits when there is a *changing* current in one of the circuits.
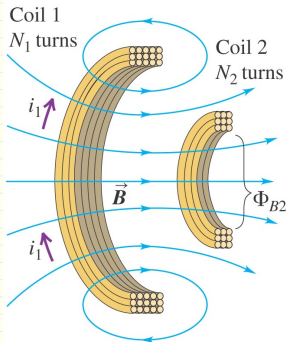
# Mutual inductance

**Mutual inductance:** If the current in coil 1 is changing, the changing flux through coil 2 induces an emf in coil 2.



- We use lowercase letters to represent quantities that vary with time (e.g.  $i$ ).
- $i_1$  produces  $B$ , according to Biot-Savarts law:

$$\vec{B} = \frac{\mu_0}{4\pi} \int \frac{i_1 d\vec{\ell} \times \hat{r}}{r^2} \Rightarrow B \propto i_1$$


- $\Phi$  through the 2nd loop is proportional to  $B$

$$\Phi_{B2} = \int \vec{B} \cdot d\vec{A} \Rightarrow \Phi_{B2} \propto B$$

- Thus  $\Phi_{B2} \propto i_1$ .
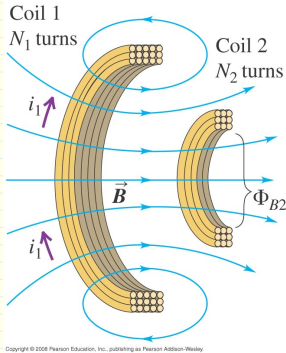
# Mutual inductance

**Mutual inductance:** If the current in coil 1 is changing, the changing flux through coil 2 induces an emf in coil 2.




- We call the proportionality constant as the *mutual inductance*,  $M_{21}$ .
- If there are  $N_2$  turns, the same flux passes through each loop, and

$$N_2 \Phi_{B2} = M_{21} i_1 \quad (1)$$

defines  $M_{21}$ .
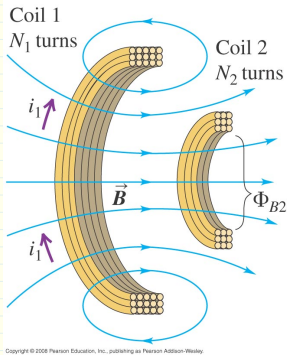
# Mutual inductance

**Mutual inductance:** If the current in coil 1 is changing, the changing flux through coil 2 induces an emf in coil 2.



- When  $i_1$  changes,  $\Phi_{B2}$  changes; this changing flux induces an emf  $\mathcal{E}_2$  in coil 2, given by

$$\mathcal{E}_2 = -N_2 \frac{d\Phi_{B2}}{dt} \quad (1)$$

Using  $N_2 \Phi_{B2} = M_{21} i_1$

$$\mathcal{E}_2 = -M_{21} \frac{di_1}{dt} \quad (2)$$



# Mutual inductance


**Mutual inductance:** If the current in coil 1 is changing, the changing flux through coil 2 induces an emf in coil 2.

- We found  $\Phi_{B2} \propto i_1$ .
- Then the mutual inductance

$$M_{21} = \frac{N_2 \Phi_{B2}}{i_1}$$


is a constant that depends only on the geometry of the two coils (the size, shape, number of turns, and orientation of each coil and the separation between the coils).

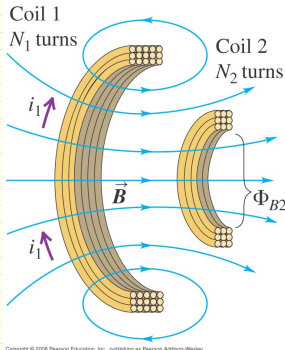- This is always valid if the coils are in vacuum.


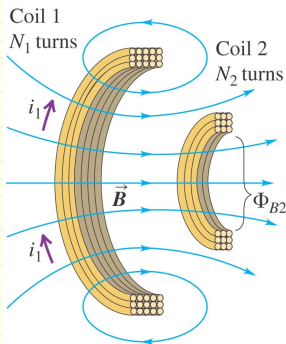
# Mutual inductance

**Mutual inductance:** If the current in coil 1 is changing, the changing flux through coil 2 induces an emf in coil 2.




Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley

- If a magnetic material is present,  $M_{21}$  also depends on the magnetic properties of the material.
- If the material has nonlinear magnetic properties—that is, if the relative permeability  $K_m$  is not constant and magnetization is not proportional to magnetic field—then  $\Phi_{B2}$  is no longer directly proportional to  $i_1$ .
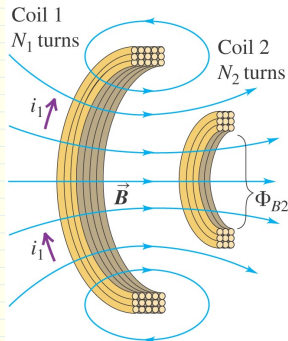
# Mutual inductance

**Mutual inductance:** If the current in coil 1 is changing, the changing flux through coil 2 induces an emf in coil 2.




- A changing current  $i_2$  in **coil 2** causes a changing flux  $\Phi_{B1}$  and an emf  $\mathcal{E}_1$  in **coil 1**.
- The corresponding constant  $M_{12} = M_{21}$  *always*, even though in general the two coils are not identical and  $\Phi$  through them is not the same.

$$M = M_{21} = \frac{N_2 \Phi_{B2}}{i_1} = M_{12} = \frac{N_1 \Phi_{B1}}{i_2} \quad (1)$$

- Mutual inductance,  $M$ , characterizes completely the induced-emf interaction of two coils.
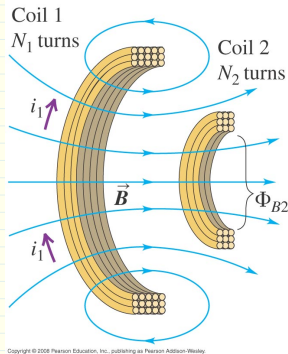
# Mutual inductance

**Mutual inductance:** If the current in coil 1 is changing, the changing flux through coil 2 induces an emf in coil 2.



Mutually induced emfs are then

$$\mathcal{E}_2 = -M \frac{di_1}{dt}, \quad \mathcal{E}_1 = -M \frac{di_2}{dt} \quad (1)$$

## Unit of inductance

- The SI unit of mutual inductance is called the *henry* ( $1\text{ H}$ )<sup>1</sup>
- One henry is equal to one weber per ampere ( $M = N_2\Phi_{B2}/i_1$ )
- Other equivalent units

$$1\text{ H} = 1\text{ Wb/A} = 1\text{ V} \cdot \text{s/A} = 1\text{ } \Omega \cdot \text{s} = 1\text{ J/A}^2 \quad (2)$$

---

<sup>1</sup>In honor of the American physicist Joseph Henry (1797-1878), one of the discoverers of electromagnetic induction.

# Drawbacks and Uses of Mutual Inductance

- Mutual inductance can be a nuisance in electric circuits, since variations in current in one circuit can induce unwanted emfs in other nearby circuits.
- To minimize these effects two coils would be placed far apart.
- Mutual inductance also has many useful applications:
- A transformer
- How do electric toothbrushes charge through plastic?

# Drawbacks and Uses of Mutual Inductance

- Mutual inductance can be a nuisance in electric circuits, since variations in current in one circuit can induce unwanted emfs in other nearby circuits.
- To minimize these effects two coils would be placed far apart.
- Mutual inductance also has many useful applications:
- A transformer
- How do electric toothbrushes charge through plastic?


# Drawbacks and Uses of Mutual Inductance

- Mutual inductance can be a nuisance in electric circuits, since variations in current in one circuit can induce unwanted emfs in other nearby circuits.
- To minimize these effects two coils would be placed far apart.
- Mutual inductance also has many useful applications:
  - A transformer
  - How do electric toothbrushes charge through plastic?



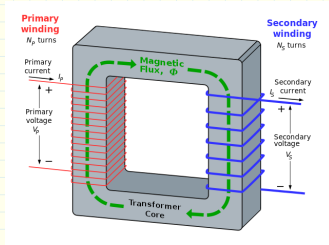
# Drawbacks and Uses of Mutual Inductance

- Mutual inductance can be a nuisance in electric circuits, since variations in current in one circuit can induce unwanted emfs in other nearby circuits.
- To minimize these effects two coils would be placed far apart.
- Mutual inductance also has many useful applications:
- A transformer
- How do electric toothbrushes charge through plastic?


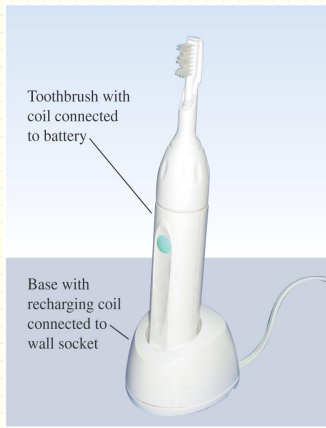
# Drawbacks and Uses of Mutual Inductance



Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley


- Mutual inductance can be a nuisance in electric circuits, since variations in current in one circuit can induce unwanted emfs in other nearby circuits.
- To minimize these effects two coils would be placed far apart.
- Mutual inductance also has many useful applications:
- A transformer
- Electric toothbrush

# Drawbacks and Uses of Mutual Inductance




- Mutual inductance can be a nuisance in electric circuits, since variations in current in one circuit can induce unwanted emfs in other nearby circuits.
- To minimize these effects two coils would be placed far apart.
- Mutual inductance also has many useful applications:
- A transformer
- How do electric toothbrushes charge through plastic?
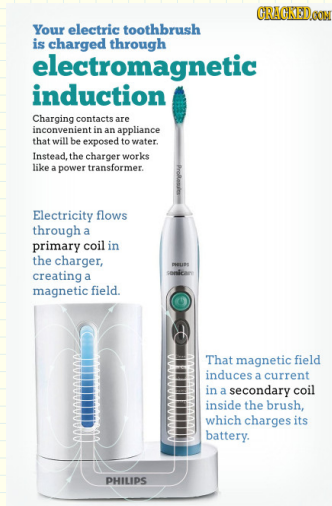
# Drawbacks and Uses of Mutual Inductance



- Mutual inductance can be a nuisance in electric circuits, since variations in current in one circuit can induce unwanted emfs in other nearby circuits.
- To minimize these effects two coils would be placed far apart.
- Mutual inductance also has many useful applications:
- A transformer
- How do electric toothbrushes charge through plastic?

## Ex: Calculating mutual inductance

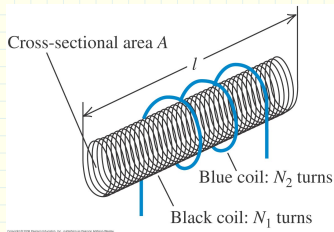

This is a form of Tesla coil  
(a high-voltage generator  
popular in science  
museums)

### Question

A long solenoid with length  $l$  and cross-sectional area  $A$  is closely wound with  $N_1$  turns of wire. A coil with  $N_2$  turns surrounds it at its center. Find the mutual inductance  $M$ .

## Ex: Calculating mutual inductance


### Solution

- $B_1$  at the center of the solenoid

$$B_1 = \mu_0 n_1 i_1 = \frac{\mu_0 N_1 i_1}{l}$$

where  $n_1 = N_1/l$ .

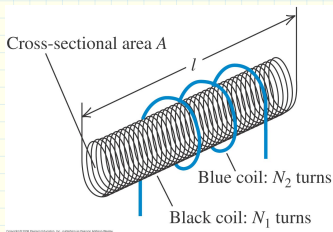- The flux through a cross section of the solenoid equals  $B_1 A$ .
- This also equals the flux  $\Phi_{B2}$  through each turn of the outer coil, independent of its cross-sectional area as there is almost no magnetic field outside a very long solenoid.




This is a form of Tesla coil  
(a high-voltage generator  
popular in science  
museums)

## Ex: Calculating mutual inductance
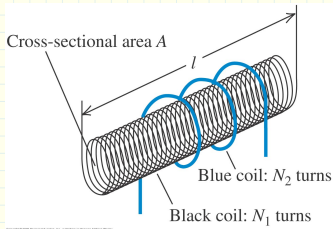
### Solution

- The mutual inductance is then


$$\begin{aligned} M &= \frac{N_2 \Phi_{B2}}{i_1} = \frac{N_2 B_1 A}{i_1} \\ &= \frac{\mu_0 N_1 N_2 A i_1}{l i_1} = \frac{\mu_0 N_1 N_2 A}{l} \end{aligned}$$



This is a form of Tesla coil  
(a high-voltage generator  
popular in science  
museums)

- The mutual inductance  $M$  of any two coils is proportional to the product  $N_1 N_2$  of their numbers of turns.
- Notice that  $M$  depends only on the geometry of the two coils, not on the current.

## Ex: Calculating mutual inductance

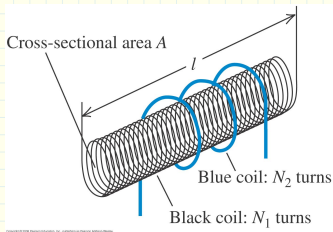

This is a form of Tesla coil  
(a high-voltage generator  
popular in science  
museums)

### Numerical

Suppose  $l = 0.50$  m,

$A = 10 \text{ cm}^2 = 1.0 \times 10^{-3} \text{ m}^2$ ,

$N_1 = 1000$  turns, and  $N_2 = 10$  turns.


The mutual inductance is then

$$\begin{aligned} M &= \frac{\mu_0 N_1 N_2 A}{l} \\ &= \frac{4\pi \times 10^{-7} \text{ Wb/A} \cdot \text{m} \times 1000 \times 10 \times 1.0 \times 10^{-3} \text{ m}^2}{0.50 \text{ m}} \\ &= 25 \times 10^{-6} \text{ H} \end{aligned}$$


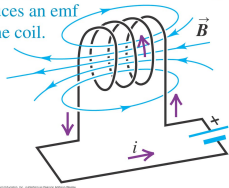
# Self-inductance


**Self-inductance:** If the current  $i$  in the coil is changing, the changing flux through the coil induces an emf in the coil.



- A current in a circuit sets up a magnetic field that causes a magnetic flux through the *same* circuit;
- this flux changes when the current changes.
- Thus any circuit that carries a varying current has an emf induced in it by the variation in its own  $B$ . Such an emf is called a *self-induced emf*.
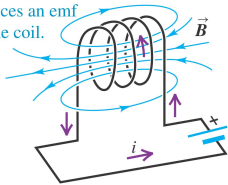
# Self-inductance

**Self-inductance:** If the current  $i$  in the coil is changing, the changing flux through the coil induces an emf in the coil.



- By *Lenz's law*, a self-induced emf opposes the change in  $i$  that caused the emf and so tends to make it more difficult for variations in  $i$  to occur.
- Self-induced emfs can occur in any circuit, since there is always some  $\Phi_B$  through the closed loop of a current-carrying circuit.
- But the effect is greatly enhanced if the circuit includes a coil with  $N$  turns of wire.

# Self-inductance

- The self-inductance of the circuit is defined as


$$L = \frac{N\Phi_B}{i} \quad (3)$$

From Faraday's law  $\mathcal{E} = -Nd\Phi_B/dt$


$$\mathcal{E} = -L \frac{di}{dt} \quad (4)$$

- The  $-$  sign is a reflection of Lenz's law: the self-induced emf in a circuit opposes any change in the current in that circuit.

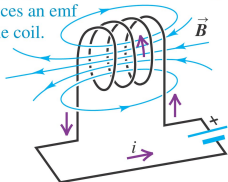**Self-inductance:** If the current  $i$  in the coil is changing, the changing flux through the coil induces an emf in the coil.



# Inductors as circuit elements


- A circuit device that is designed to have a particular inductance is called an inductor, or a choke.
- The usual circuit symbol for an inductor is 
- Their purpose is to oppose any variations in the current through the circuit.

## Application



- If lightning strikes part of an electrical power transmission system, it causes a sudden spike in voltage that can damage the components of the system as well as anything connected to that system.
- To minimize these effects, large inductors are incorporated into the transmission system.
- An inductor opposes and suppresses any rapid changes in the current.


# Self-inductance of an ideal soleoid

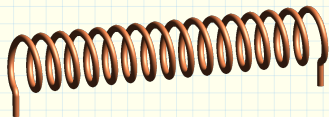

- Prototype of inductors.
- $n = N/l$
- $B = \mu_0 n i$
- $\Phi_B = BA = \mu_0 n i A$
- Then

$$L = \frac{N\Phi_B}{i} = \mu_0 n N A$$


# Self-inductance of an ideal soleoid

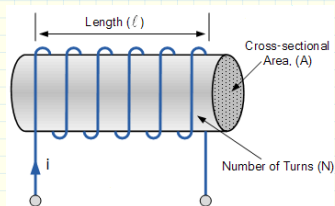

- Prototype of inductors.
- $n = N/l$
- $B = \mu_0 ni$
- $\Phi_B \equiv BA \equiv \mu_0 niA$
- Then

$$L = \frac{N\Phi_B}{i} = \mu_0 nNA$$

# Self-inductance of an ideal soleoid

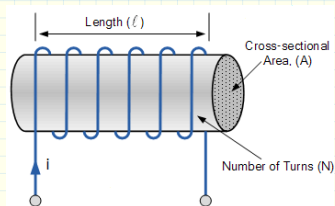


- Prototype of inductors.
- $n = N/l$
- $B = \mu_0 ni$
- $\Phi_B \equiv BA \equiv \mu_0 niA$
- Then

$$L = \frac{N\Phi_B}{i} = \mu_0 nNA$$




# Self-inductance of an ideal soleoid

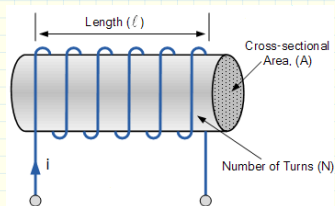

- Prototype of inductors.
- $n = N/l$
- $B = \mu_0 n i$
- $\Phi_B = BA = \mu_0 n i A$
- Then

$$L = \frac{N\Phi_B}{i} = \mu_0 n N A$$

## Self-inductance of an ideal soleoid

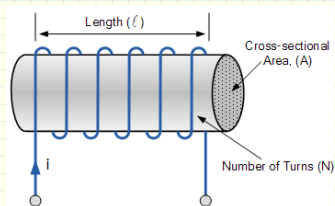

- Prototype of inductors.
- $n = N/\ell$
- $B = \mu_0 n i$
- $\Phi_B = BA = \mu_0 n i A$
- Then


$$L = \frac{N\Phi_B}{i} = \mu_0 n N A$$

## Self-inductance of a toroidal soleoid




- $B = \frac{\mu_0 Ni}{2\pi r}$
- $\Phi_B = \int \vec{B} \cdot d\vec{A} = \int_a^b Bh \, dr = \frac{\mu_0 Nih}{2\pi} \ln \frac{b}{a}$
- $L = \frac{N\Phi_B}{i} = \frac{\mu_0 N^2 h}{2\pi} \ln \frac{b}{a}$

## Self-inductance of a toroidal soleoid

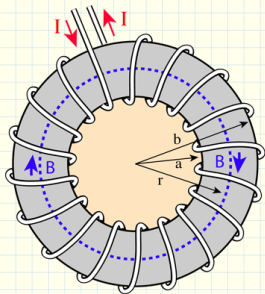


- $B = \frac{\mu_0 Ni}{2\pi r}$
- $\Phi_B = \int \vec{B} \cdot d\vec{A} = \int_a^b Bh \, dr = \frac{\mu_0 Nih}{2\pi} \ln \frac{b}{a}$
- $L = \frac{N\Phi_B}{i} = \frac{\mu_0 N^2 h}{2\pi} \ln \frac{b}{a}$

## Self-inductance of a toroidal soleoid

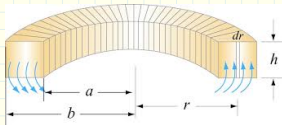

- $B = \frac{\mu_0 Ni}{2\pi r}$
- $\Phi_B = \int \vec{\mathbf{B}} \cdot d\vec{\mathbf{A}} = \int_a^b Bh \, dr = \frac{\mu_0 Nih}{2\pi} \ln \frac{b}{a}$
- $L = \frac{N\Phi_B}{i} = \frac{\mu_0 N^2 h}{2\pi} \ln \frac{b}{a}$


## Self-inductance of a toroidal soleoid

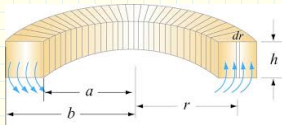


- $B = \frac{\mu_0 Ni}{2\pi r}$
- $\Phi_B = \int \vec{\mathbf{B}} \cdot d\vec{\mathbf{A}} = \int_a^b Bh \, dr = \frac{\mu_0 Nih}{2\pi} \ln \frac{b}{a}$
- $L = \frac{N\Phi_B}{i} = \frac{\mu_0 N^2 h}{2\pi} \ln \frac{b}{a}$
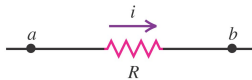
# Magnetic field energy

Resistor with current  $i$ : energy is *dissipated*.



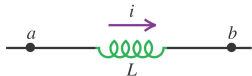
Inductor with current  $i$ : energy is *stored*.




- An inductor carrying a current has energy stored in it.
- Establishing a current in an inductor requires an input of energy.
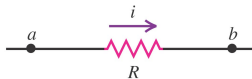
# Energy Stored in an Inductor

Resistor with current  $i$ : energy is *dissipated*.



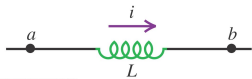Inductor with current  $i$ : energy is *stored*.



- What is the total energy input  $U$  needed to establish a final current  $I$  in an inductor with inductance  $L$  if the initial current is zero.
- The rate  $P$  at which energy is being delivered to the inductor is

$$P = V_{ab}i = L \frac{di}{dt}i$$




# Energy Stored in an Inductor


- The energy  $dU$  supplied to the inductor during an infinitesimal time interval  $dt$  is  $dU = Pdt$ , so

$$dU = Li di$$

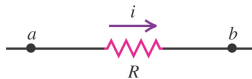Resistor with current  $i$ : energy is *dissipated*.



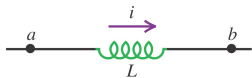Inductor with current  $i$ : energy is *stored*.



- The total energy  $U$  supplied while the current increases from zero to a final value  $I$  is

$$U = L \int_0^I i di = \frac{1}{2} LI^2$$

- Where is this energy stored?

# Magnetic energy density

- The magnetic energy density

## Recall

- The electric energy density was defined as

$$u_E = \frac{1}{2}\epsilon_0 E^2$$

- The energy given to a capacitor was stored in the electric field

$$u_B = \frac{B^2}{2\mu_0} \quad (5)$$

- Ex: The magnetic energy density in an ideal solenoid is then
$$u_B = \frac{(\mu_0 n i)^2}{2\mu_0} = \frac{1}{2}\mu_0 n^2 i^2$$
- The energy in an ideal solenoid is then  $U_B = u_B A l = \frac{1}{2}\mu_0 n^2 l A i^2$
- Recalling  $L = \mu_0 n^2 l A$  we get  $U_B = \frac{1}{2} L i^2 = U$ .
- All given energy is stored in the magnetic field.

# Magnetic energy density

- The magnetic energy density

## Recall

- The electric energy density was defined as

$$u_E = \frac{1}{2}\epsilon_0 E^2$$

- The energy given to a capacitor was stored in the electric field

$$u_B = \frac{B^2}{2\mu_0} \quad (5)$$

- Ex: The magnetic energy density in an ideal solenoid is then
$$u_B = \frac{(\mu_0 ni)^2}{2\mu_0} = \frac{1}{2}\mu_0 n^2 i^2$$
- The energy in an ideal solenoid is then  $U_B = u_B A l = \frac{1}{2}\mu_0 n^2 l A i^2$
- Recalling  $L = \mu_0 n^2 l A$  we get
$$U_B = \frac{1}{2} L i^2 = U.$$
- All given energy is stored in the magnetic field.

## Energy stored in a toroidal solenoid

- Recall  $L = \frac{N\Phi}{i} = \frac{\mu_0 N^2 h}{2\pi} \ln \frac{b}{a}$  and so

$$U = \frac{1}{2} Li^2 = \frac{\mu_0 N^2 h}{4\pi} \ln \frac{b}{a} i^2$$

- Let us find this from the energy density.
- Recall  $B = \mu_0 Ni / 2\pi r$
- Energy density:  $u_B = B^2 / 2\mu_0 = \mu_0 N^2 i^2 / 8\pi^2 r^2$  (not uniform)
- Consider a cylindrical shell of radius  $r$ , thickness  $dr$  and height  $h$ . It's volume is  $dV = 2\pi r dr h$ . The energy stored is  $dU = u_B dV$

$$\begin{aligned} U_B &\equiv \int_a^b u_B dV = \int_a^b \frac{\mu_0 N^2 i^2}{8\pi^2 r^2} 2\pi r dr h \\ &= \frac{\mu_0 N^2 h i^2}{4\pi} \int_a^b \frac{dr}{r} \\ &= \frac{\mu_0 N^2 h i^2}{4\pi} \ln \frac{b}{a} = U \end{aligned}$$

## Energy stored in a toroidal solenoid

- Recall  $L = \frac{N\Phi}{i} = \frac{\mu_0 N^2 h}{2\pi} \ln \frac{b}{a}$  and so

$$U = \frac{1}{2} Li^2 = \frac{\mu_0 N^2 h}{4\pi} \ln \frac{b}{a} i^2$$

- Let us find this from the energy density.
- Recall  $B = \mu_0 Ni / 2\pi r$
- Energy density:  $u_B = B^2 / 2\mu_0 = \mu_0 N^2 i^2 / 8\pi^2 r^2$  (not uniform)
- Consider a cylindrical shell of radius  $r$ , thickness  $dr$  and height  $h$ . It's volume is  $dV = 2\pi r dr h$ . The energy stored is  $dU = u_B dV$

$$\begin{aligned} U_B &\equiv \int_a^b u_B dV = \int_a^b \frac{\mu_0 N^2 i^2}{8\pi^2 r^2} 2\pi r dr h \\ &= \frac{\mu_0 N^2 h i^2}{4\pi} \int_a^b \frac{dr}{r} \\ &= \frac{\mu_0 N^2 h i^2}{4\pi} \ln \frac{b}{a} = U \end{aligned}$$

## Energy stored in a toroidal solenoid

- Recall  $L = \frac{N\Phi}{i} = \frac{\mu_0 N^2 h}{2\pi} \ln \frac{b}{a}$  and so

$$U = \frac{1}{2} Li^2 = \frac{\mu_0 N^2 h}{4\pi} \ln \frac{b}{a} i^2$$

- Let us find this from the energy density.
- Recall  $B = \mu_0 Ni / 2\pi r$
- Energy density:  $u_B = B^2 / 2\mu_0 = \mu_0 N^2 i^2 / 8\pi^2 r^2$  (not uniform)
- Consider a cylindrical shell of radius  $r$ , thickness  $dr$  and height  $h$ . It's volume is  $dV = 2\pi r dr h$ . The energy stored is  $dU = u_B dV$

$$\begin{aligned} U_B &\equiv \int_a^b u_B dV = \int_a^b \frac{\mu_0 N^2 i^2}{8\pi^2 r^2} 2\pi r dr h \\ &= \frac{\mu_0 N^2 h i^2}{4\pi} \int_a^b \frac{dr}{r} \\ &= \frac{\mu_0 N^2 h i^2}{4\pi} \ln \frac{b}{a} = U \end{aligned}$$

## Energy stored in a toroidal solenoid

- Recall  $L = \frac{N\Phi}{i} = \frac{\mu_0 N^2 h}{2\pi} \ln \frac{b}{a}$  and so

$$U = \frac{1}{2} Li^2 = \frac{\mu_0 N^2 h}{4\pi} \ln \frac{b}{a} i^2$$

- Let us find this from the energy density.
- Recall  $B = \mu_0 Ni / 2\pi r$
- Energy density:  $u_B = B^2 / 2\mu_0 = \mu_0 N^2 i^2 / 8\pi^2 r^2$  (not uniform)
- Consider a cylindrical shell of radius  $r$ , thickness  $dr$  and height  $h$ . It's volume is  $dV = 2\pi r dr h$ . The energy stored is  $dU = u_B dV$

$$\begin{aligned} U_B &\equiv \int_a^b u_B dV = \int_a^b \frac{\mu_0 N^2 i^2}{8\pi^2 r^2} 2\pi r dr h \\ &= \frac{\mu_0 N^2 h i^2}{4\pi} \int_a^b \frac{dr}{r} \\ &= \frac{\mu_0 N^2 h i^2}{4\pi} \ln \frac{b}{a} = U \end{aligned}$$

## Energy stored in a toroidal solenoid

- Recall  $L = \frac{N\Phi}{i} = \frac{\mu_0 N^2 h}{2\pi} \ln \frac{b}{a}$  and so

$$U = \frac{1}{2} Li^2 = \frac{\mu_0 N^2 h}{4\pi} \ln \frac{b}{a} i^2$$

- Let us find this from the energy density.
- Recall  $B = \mu_0 Ni / 2\pi r$
- Energy density:  $u_B = B^2 / 2\mu_0 = \mu_0 N^2 i^2 / 8\pi^2 r^2$  (not uniform)
- Consider a cylindrical shell of radius  $r$ , thickness  $dr$  and height  $h$ . Its volume is  $dV = 2\pi r dr h$ . The energy stored is  $dU = u_B dV$

$$\begin{aligned} U_B &\equiv \int_a^b u_B dV = \int_a^b \frac{\mu_0 N^2 i^2}{8\pi^2 r^2} 2\pi r dr h \\ &= \frac{\mu_0 N^2 h i^2}{4\pi} \int_a^b \frac{dr}{r} \\ &= \frac{\mu_0 N^2 h i^2}{4\pi} \ln \frac{b}{a} = U \end{aligned}$$



## Energy stored in a toroidal solenoid

- Recall  $L = \frac{N\Phi}{i} = \frac{\mu_0 N^2 h}{2\pi} \ln \frac{b}{a}$  and so


$$U = \frac{1}{2} Li^2 = \frac{\mu_0 N^2 h}{4\pi} \ln \frac{b}{a} i^2$$

- Let us find this from the energy density.
- Recall  $B = \mu_0 Ni / 2\pi r$
- Energy density:  $u_B = B^2 / 2\mu_0 = \mu_0 N^2 i^2 / 8\pi^2 r^2$  (not uniform)
- Consider a cylindrical shell of radius  $r$ , thickness  $dr$  and height  $h$ . It's volume is  $dV = 2\pi r dr h$ . The energy stored is  $dU = u_B dV$

$$\begin{aligned} U_B &= \int_a^b u_B dV = \int_a^b \frac{\mu_0 N^2 i^2}{8\pi^2 r^2} 2\pi r dr h \\ &= \frac{\mu_0 N^2 h i^2}{4\pi} \int_a^b \frac{dr}{r} \\ &= \frac{\mu_0 N^2 h i^2}{4\pi} \ln \frac{b}{a} = U \end{aligned}$$
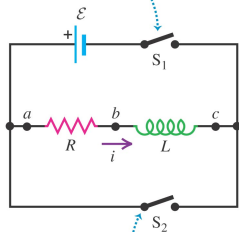
## The $R - L$ circuit

Closing switch  $S_1$  connects the  $R$ - $L$  combination in series with a source of emf  $\mathcal{E}$ .




Closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.


- How does an inductor behave in a circuit?
- An inductor in a circuit makes it difficult for rapid changes in current to occur, thanks to the effects of self-induced emf.
- According to  $\mathcal{E} = -L \frac{di}{dt}$  the greater the rate of change of current  $\frac{di}{dt}$ , the greater the self-induced emf and the greater the potential difference between the inductor terminals.

# The potential difference across an inductor

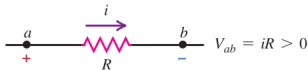
(a) Resistor with current  $i$  flowing from  $a$  to  $b$ : potential drops from  $a$  to  $b$ .



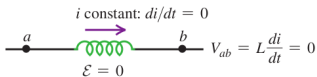
(b) Inductor with *constant* current  $i$  flowing from  $a$  to  $b$ : no potential difference.



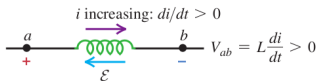(c) Inductor with *increasing* current  $i$  flowing from  $a$  to  $b$ : potential drops from  $a$  to  $b$ .



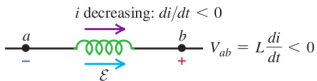
(d) Inductor with *decreasing* current  $i$  flowing from  $a$  to  $b$ : potential increases from  $a$  to  $b$ .



- The potential difference across a resistor depends on the current (a).
- whereas the potential difference across an inductor depends on the rate of change of the current (b), (c), (d) .

## The $R - L$ circuit

Switch  $S_1$  is closed at  $t = 0$ .

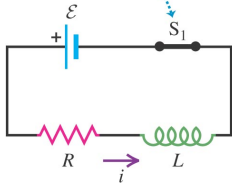


- Apply Kirchhoff's loop rule

$$\mathcal{E} - iR - L \frac{di}{dt} = 0$$

- Arrange


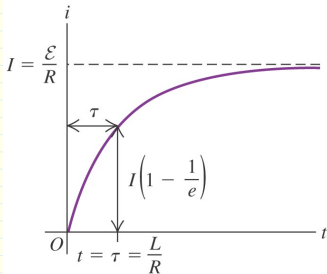
$$\frac{di}{i - (\mathcal{E}/R)} = -\frac{R}{L} dt$$



Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley

# The $R - L$ circuit

Switch  $S_1$  is closed at  $t = 0$ .

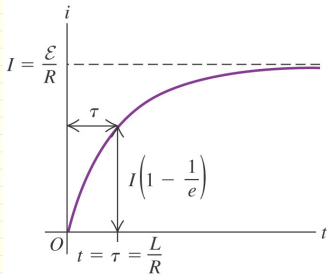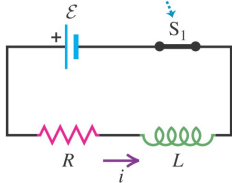

Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley

- Integrate


$$\int_0^i \frac{di'}{i' - (\mathcal{E}/R)} = - \int_0^t \frac{R}{L} dt'$$
$$\ln \left( \frac{i - (\mathcal{E}/R)}{-\mathcal{E}/R} \right) = - \frac{R}{L} t$$

- take exponentials of both sides and solve for  $i$

$$i = \frac{\mathcal{E}}{R} \left( 1 - e^{-t/\tau} \right), \quad \tau = L/R$$

# The $R - L$ circuit

Switch  $S_1$  is closed at  $t = 0$ .

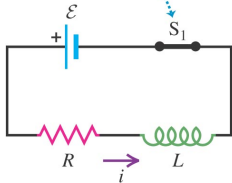


- Recall

$$i = \frac{\mathcal{E}}{R} \left( 1 - e^{-t/\tau} \right)$$

- Take derivative:


$$\frac{di}{dt} = \frac{\mathcal{E}}{L} e^{-t/\tau}$$

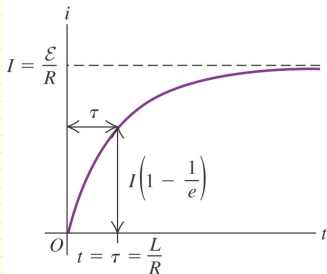- At time  $t = 0$ ,  $i = 0$  and  $di/dt = \mathcal{E}/L$ . As  $t \rightarrow \infty$ ,  $i \rightarrow \mathcal{E}/R$  and  $di/dt \rightarrow 0$



Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley

## The $R - L$ circuit

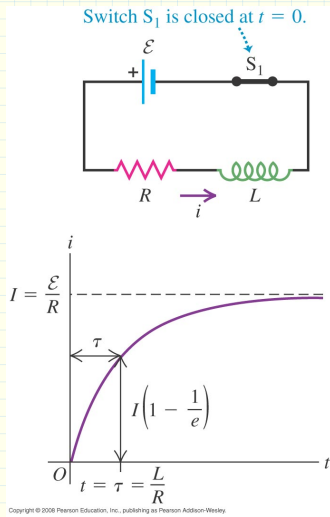

- Recall

$$i = \frac{\mathcal{E}}{R} \left(1 - e^{-t/\tau}\right)$$


- At  $t = \tau$  the current has risen to  $(1 - 1/e) \simeq 63\%$  of its final value.
- At  $t = 5\tau$  the current has risen to  $99.3\%$  of its final value.

## Energy considerations

- The rate at which the source delivers energy to the circuit is  $P_{\mathcal{E}} = \mathcal{E}i$ .
- The rate at which energy is dissipated in the resistor is  $P_R = i^2R$ .
- The rate at which energy is stored in the inductor is  $P_L = Li \frac{di}{dt}$
- Multiply  $\mathcal{E} - iR - L \frac{di}{dt} = 0$  by  $i$  and arrange

$$\mathcal{E}i = i^2R + Li \frac{di}{dt}$$

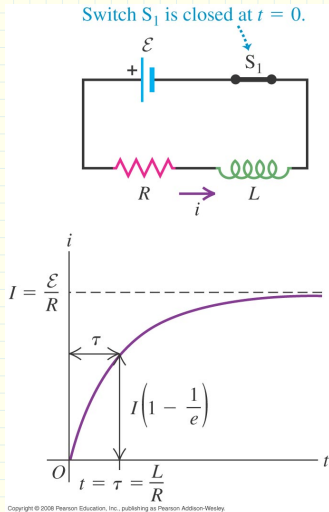Of the power supplied by the source  $\mathcal{E}i$ , part  $i^2R$  is dissipated in  $R$  and part  $Li \frac{di}{dt}$  goes to store energy in  $L$ .





# Energy delivered by the source


- The rate at which the source delivers energy to the circuit is  $P_{\mathcal{E}} = \mathcal{E}i$ .
- $dU_{\mathcal{E}} = P_{\mathcal{E}}dt$  and  $i = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau})$
- $U_{\mathcal{E}} = \int_0^{\infty} \mathcal{E}i dt$

$$U_{\mathcal{E}} = \frac{\mathcal{E}^2}{R} \int_0^{\infty} (1 - e^{-t/\tau}) dt$$

$$= \frac{\mathcal{E}^2}{R} \tau \int_0^{\infty} (1 - e^{-x}) dx$$


where  $x \equiv t/\tau$ . The integral diverges. If we integrate to some finite  $x_f \gg 1$
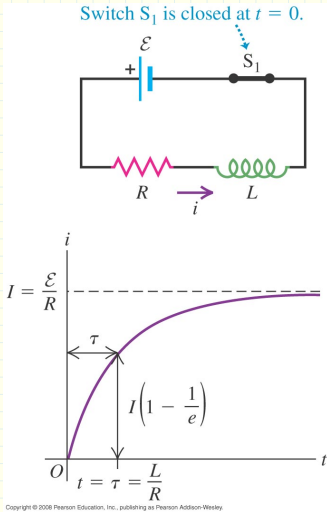
$$U_{\mathcal{E}} = \frac{\mathcal{E}^2}{R} \tau (x + e^{-x})_0^{x_f} \simeq \frac{\mathcal{E}^2}{R} \tau (x_f - 1)$$


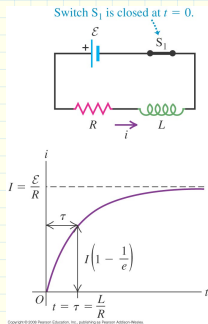
## Energy dissipated on the resistor

- The rate at which the resistor dissipates energy is  $P_R = Ri^2$ .
- $dU_R = P_R dt$  and  $i = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau})$
- $U_R = R \int_0^\infty i^2 dt$



$$U_R = \frac{\mathcal{E}^2}{R} \int_0^\infty (1 - e^{-t/\tau})^2 dt$$
$$= \frac{\mathcal{E}^2}{R} \tau \int_0^\infty (1 - e^{-x})^2 dx$$

where  $x \equiv t/\tau$ . If we integrate to some finite  $x_f \gg 1$

$$U_R = \frac{\mathcal{E}^2}{R} \tau \left( x + 2e^{-x} - \frac{1}{2}e^{-2x} \right)_0^{x_f} \simeq \frac{\mathcal{E}^2}{R} \tau (x_f - \frac{3}{2})$$


## Energy stored on the inductor

- The rate at which the inductor stores energy is  $P_L = L di/dt$ .
- $dU_L = P_L dt$  and  $i = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau})$ ,  
 $di/dt = \frac{\mathcal{E}}{R\tau} e^{-t/\tau}$
- $U_L = L \int_0^\infty i(di/dt) dt$

$$\begin{aligned} U_L &= L \frac{\mathcal{E}^2}{R^2 \tau} \int_0^\infty (1 - e^{-t/\tau}) e^{-t/\tau} dt \\ &= \frac{\mathcal{E}^2}{R} \tau \int_0^\infty (1 - e^{-x}) e^{-x} dx \end{aligned}$$

where  $x \equiv t/\tau$ . If we integrate to some finite  $x_f \gg 1$
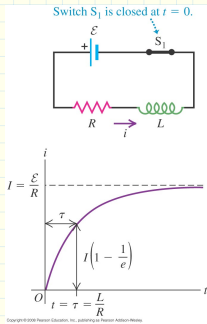
$$U_L = \frac{\mathcal{E}^2}{R} \tau \frac{1}{2} ((1 - e^{-x})^2)_0^{x_f} \simeq \frac{\mathcal{E}^2}{2R} \tau = \frac{1}{2} LI^2$$



## In summary

- Energy delivered by the source to the circuit

$$U_{\mathcal{E}} \simeq \frac{\mathcal{E}^2}{R} \tau (x_f - 1)$$


- Energy dissipated on the resistor

$$U_R \simeq \frac{\mathcal{E}^2}{R} \tau \left( x_f - \frac{3}{2} \right)$$

- Energy stored on the inductor


$$U_L \simeq \frac{\mathcal{E}^2}{R} \tau \frac{1}{2}$$

- $U_{\mathcal{E}} = U_R + U_L$

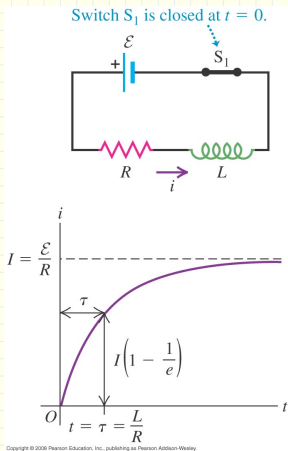

Since the current does not go to zero, there is always some dissipation of energy on the resistor which is supplied by the source.

## Current decay in an R-L circuit

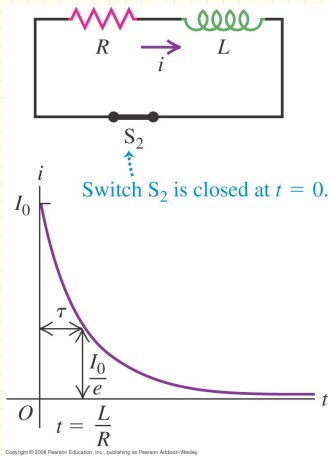

- Now suppose switch  $S_1$  has been closed for a while and the current has reached the value  $I_0$ .
- We reset our stopwatch to redefine the initial time, we close switch  $S_2$  at time  $t = 0$ , bypassing the battery.
- Kirchhoff's loop eqn:  
 $-iR - L\frac{di}{dt} = 0$  whose solution is


$$i = I_0 e^{-t/\tau}, \quad \tau = L/R \quad (6)$$

## Ex: $R - L$ circuit


### Question

An inductor with inductance  $L = 0.300 \text{ H}$  and negligible resistance is connected to a battery, a switch  $S$ , and two resistors,  $R_1 = 12.0 \Omega$  and  $R_2 = 16.0 \Omega$ . The battery has emf  $96.0 \text{ V}$  and negligible internal resistance.  $S$  is closed at  $t = 0$ .

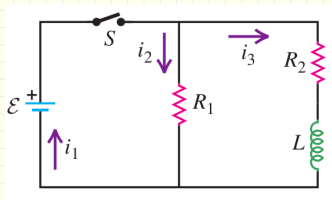(a) What are the currents  $i_1$ ,  $i_2$ , and  $i_3$  just after  $S$  is closed? (b) What are  $i_1$ ,  $i_2$ , and  $i_3$  after  $S$  has been closed a long time?




## Ex: $R - L$ circuit

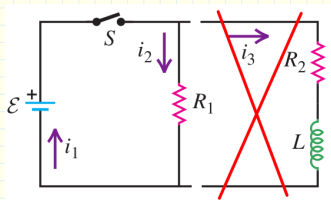

### Solution a

- As soon as the  $S$  is closed there is no current on the  $L$  branch.
- $i_3 = 0$
- $i_1 = i_2 = \mathcal{E}/R_1$

## Ex: $R - L$ circuit

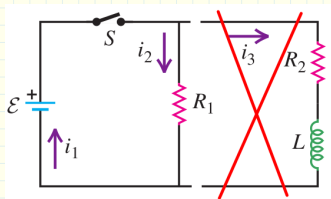


### Solution a

- As soon as the  $S$  is closed there is no current on the  $L$  branch.
- $i_3 = 0$
- $i_1 = i_2 = \mathcal{E}/R_1$



## Ex: $R - L$ circuit

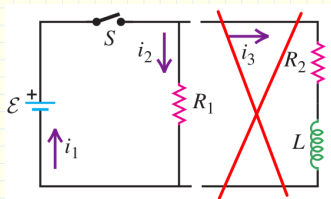

### Solution a


- As soon as the  $S$  is closed there is no current on the  $L$  branch.
- $i_3 = 0$
- $i_1 = i_2 = \mathcal{E}/R_1$

## Ex: $R - L$ circuit
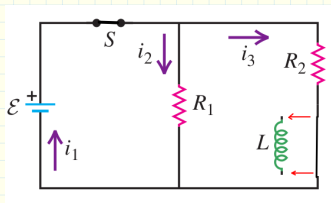
### Solution b

- After  $S$  has been closed a long time  $L$  acts just like a wire (as  $di/dt = 0$ ).


- $i_2 = \mathcal{E}/R_1$
- $i_3 = \mathcal{E}/R_2$
- $i_1 = i_2 + i_3$



## Ex: $R - L$ circuit
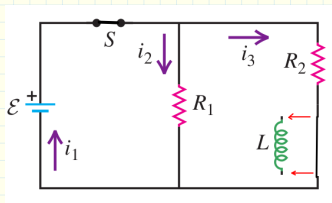
### Solution b


- After  $S$  has been closed a long time  $L$  acts just like a wire (as  $di/dt = 0$ ).
- $i_2 = \mathcal{E}/R_1$
- $i_3 = \mathcal{E}/R_2$
- $i_1 = i_2 + i_3$



## Ex: $R - L$ circuit
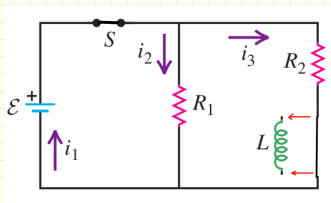
### Solution b

- After  $S$  has been closed a long time  $L$  acts just like a wire (as  $di/dt = 0$ ).
- $i_2 = \mathcal{E}/R_1$
- $i_3 = \mathcal{E}/R_2$
- $i_1 = i_2 + i_3$



## Ex: $R - L$ circuit

### Solution b

- After  $S$  has been closed a long time  $L$  acts just like a wire (as  $di/dt = 0$ ).
- $i_2 = \mathcal{E}/R_1$
- $i_3 = \mathcal{E}/R_2$
- $i_1 = i_2 + i_3$

