

Advanced Digital Circuit Design - State Reduction and Assignment


Prof. Dr. Berna Örs Yalçın

Istanbul Technical University
Faculty of Electrical and Electronics Engineering
Department of Electronics and Communication
Engineering
siddika.ors@itu.edu.tr

State Reduction and Assignment

- In the design process of sequential circuits certain techniques are useful in reducing the circuit complexity
 - state reduction
 - state assignment
- State reduction
 - Fewer states \rightarrow fewer number of flip-flops
 - m flip-flops $\rightarrow 2^m$ states
 - Example: $m = 5 \rightarrow 2^m = 32$
 - If we reduce the number of states to 21 do we reduce the number of flip-flops?

Example: State Reduction

 


Note that we use letters to designate the states for the time being

Example: State Reduction

state	a	a	b	c	f	g	f	f	g	a	a		
input	0	1	0	1	0	1	1	0	0	0	0		
output	0	0	0	0	0	1	1	0	0	0			

- What is important
 - not the states
 - but the output values the circuit generates
- Therefore, the problem is to find a circuit
 - with fewer number of states,
 - but that produces the same output pattern for any given input pattern, starting with the same initial state

State Reduction Technique 1/7

 

- Step 1: get the state table

present state	next state		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	c	f	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

State Reduction Technique 2/7

- Step 2: Inspect the state table for equivalent states
 - Equivalent states: Two states,
 1. that produce exactly the same output
 - for each input combination
 2. whose next states are identical
 - for each input combination

State Reduction Technique 3/7

present state	next state		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	c	f	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

- States "e" and "g" are equivalent
- One of them can be removed

State Reduction Technique 4/7

present state	next state		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	c	d	0	0
c	c	f	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1

- We keep looking for equivalent states

State Reduction Technique 5/7

present state	next state		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	c	d	0	0
c	c	d	0	0
d	e	d	0	1
e	a	d	0	1


- We keep looking for equivalent states

State Reduction Technique 6/7

present state	next state		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	b	d	0	0
d	e	d	0	1
e	a	d	0	1

- We stop when there are no equivalent states

State Reduction Technique 7/7

 

present state	next state		Output	
	x = 0	x = 1	x = 0	x = 1
a	a	b	0	0
b	b	d	0	0
d	e	d	0	1
e	a	d	0	1


We need two flip-flops

state	a	a	b	b	d	e	d	d	e	a	a		
input	0	1	0	1	0	1	1	0	0	0	0		
output	0	0	0	0	0	1	1	0	0	0			11

Implication Tables

- A procedure for finding all the equivalent states in a state table.
- Use an implication table - a chart that has a square for each pair of states.


Present State	Next State		Present Output
	X = 0	1	
a	d	c	0
b	f	h	0
c	e	d	1
d	a	e	0
e	c	a	1
f	f	b	1
g	b	h	0
h	c	g	1

 

Step 1

- Use a X in the square to eliminate output incompatible states.
- 1st output of a differs from c, e, f, and h


Present State	Next State		Present Output
	X = 0	1	
a	d	c	0
b	f	h	0
c	e	d	1
d	a	e	0
e	c	a	1
f	f	b	1
g	b	h	0
h	c	g	1

 

Step 1 continued

- Continue to remove output incompatible states


Present State	Next State		Present Output
	X = 0	1	
a	d	c	0
b	f	h	0
c	e	d	1
d	a	e	0
e	c	a	1
f	f	b	1
g	b	h	0
h	c	g	1

 

Now what?

- *Implied pair* are now entered into each non X square.
- Here $a \equiv b$ iff $d \equiv f$ and $c \equiv h$


Present State	Next State		Present Output
	X = 0	1	
a	d	c	0
b	f	h	0
c	e	d	1
d	a	e	0
e	c	a	1
f	f	b	1
g	b	h	0
h	c	g	1

 

Self redundant pairs



- Self redundant pairs are removed, i.e., in square a-d it contains a-d.

Present State	Next State		Present Output
	X = 0	1	
a	d	c	0
b	f	h	0
c	e	d	1
d	a	e	0
e	c	a	1
f	f	b	1
g	b	h	0
h	c	g	1

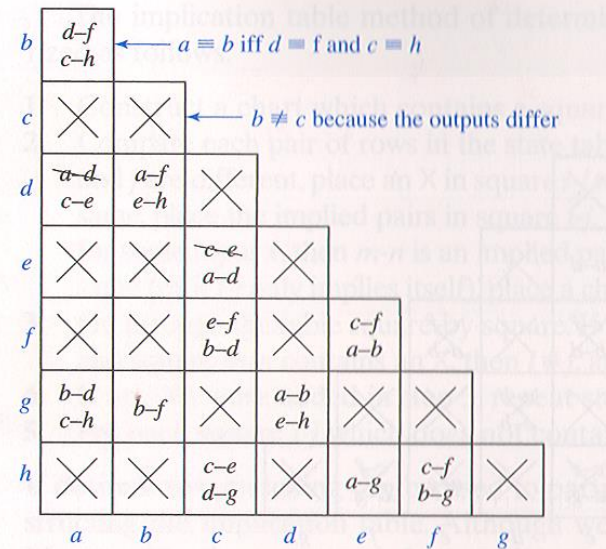

Next pass

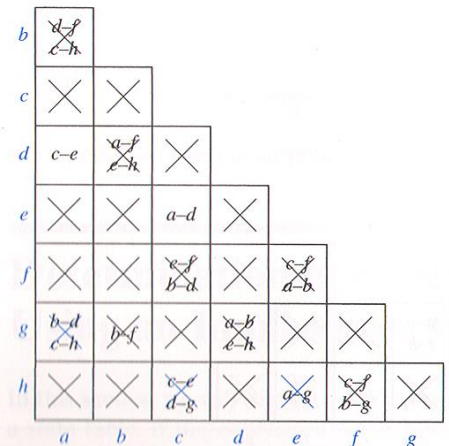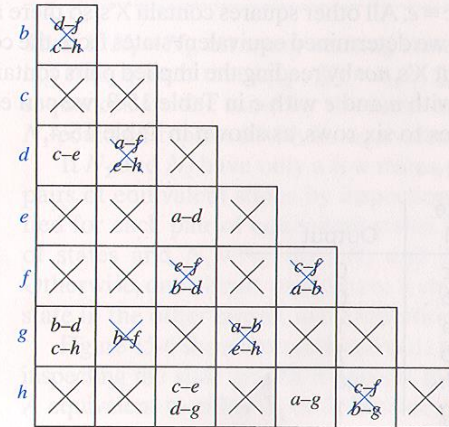- X all squares with implied pairs that are not compatible.
- Such as in a-b have d-f which has an X in it.
- Run through the chart until no further X's are found.



Final step

- Note that $a-d$ is not Xed - can conclude that $a \equiv d$. The same for $c-e$, i.e., $c \equiv e$.

<i>b</i>	$a-f$ $c-h$					
<i>c</i>	X	X				
<i>d</i>	$c-e$	$a-f$ $e-h$	X			
<i>e</i>	X	X	$a-d$	X		
<i>f</i>	X	X	$e-f$ $b-d$	X	$e-f$ $d-b$	
<i>g</i>	$b-d$ $c-h$	$b-f$	X	$a-b$ $e-h$	X	X
<i>h</i>	X	X	$c-e$ $d-g$	X	$a-g$	$c-f$ $b-g$
	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i> <i>g</i>

Reduced table

- Removing equivalent states.


Present State	Next State		Present Output
	X = 0	1	
a	d	c	0
b	f	h	0
c	e	d	1
d	a	e	0
e	c	a	1
f	f	b	1
g	b	h	0
h	c	g	1

Present State	Next State		Output
	X = 0	1	
a	a	c	0
b	f	h	0
c	c	a	1
f	f	b	1
g	b	h	0
h	c	g	1

Summary of method

1. Construct a chart with a square for each pair of states.
2. Compare each pair of rows in the state table. X a square if the outputs are different. If the output is the same enter the implied pairs.
3. Remove redundant pairs. If the implied pair is the same place a check mark as $i \equiv j$.
4. Go through the implied pairs and X the square when an implied pair is incompatible.
5. Repeat until no more Xs are added.
6. For any remaining squares not Xed, $i \equiv j$.

Another example

 


Present State	NEXT STATE		OUTPUT	
	X=0	X=1	X=0	X=1
S0	S1	S4	0	0
S1	S1	S2	0	0
S2	S3	S4	1	0
S3	S5	S2	0	0
S4	S3	S4	0	0
S5	S1	S2	0	1

Set up Implication Chart

- And remove output incompatible states

Present State	NEXT STATE		OUTPUT	
	X=0	X=1	X=0	X=1
S0	S1	S4	0	0
S1	S1	S2	0	0
S2	S3	S4	1	0
S3	S5	S2	0	0
S4	S3	S4	0	0
S5	S1	S2	0	1

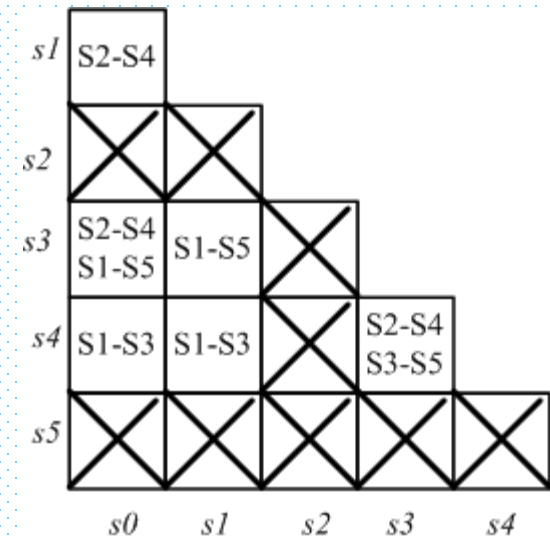



- Also indicate implied pairs

Step 2

- Check implied pairs and X
- 1st pass


and

2nd pass

  


What does it tell you?

 - In this case, the state table is minimal as no state reduction can be done.



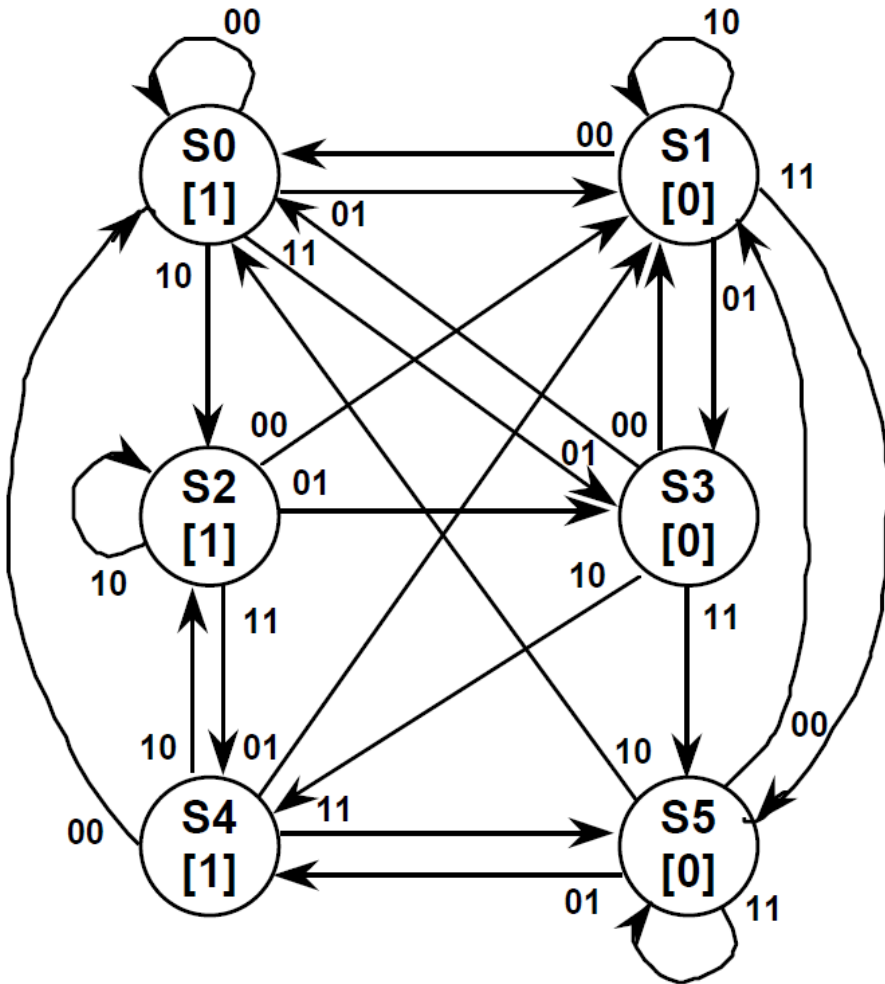State Reduction: Multiple Input State Diagram Example (1/)




State Diagram

Present State	Next State				Output
	00	01	10	11	
S ₀	S ₀	S ₁	S ₂	S ₃	1
S ₁	S ₀	S ₃	S ₁	S ₅	0
S ₂	S ₁	S ₃	S ₂	S ₄	1
S ₃	S ₁	S ₀	S ₄	S ₅	0
S ₄	S ₀	S ₁	S ₂	S ₅	1
S ₅	S ₁	S ₄	S ₀	S ₅	0

State Table

 State Reduction: Multiple Input State Diagram Example (2/)



Present State	Next State				Output
	00	01	10	11	
S_0	S_0	S_1	S_2	S_3	1
S_1	S_0	S_3	S_1	S_5	0
S_2	S_1	S_3	S_2	S_4	1
S_3	S_1	S_0	S_4	S_5	0
S_4	S_0	S_1	S_2	S_5	1
S_5	S_1	S_4	S_0	S_5	0

Present State	Next State				Output
	00	01	10	11	
S'_0	S'_0	S_1	S_2	S'_3	1
S_1	S'_0	S'_3	S_1	S'_3	0
S_2	S_1	S'_3	S_2	S'_0	1
S'_3	S_1	S'_0	S'_0	S'_3	0


Minimised State Table ₂₆

State Assignments

- We have to assign binary values to each state
- If we have m states, then we need codes of n bits, where $n = \lceil \log_2 m \rceil$
- There are different ways of encoding
- Example: Five states: S_0, S_1, S_2, S_3, S_4

state	binary	gray	one-hot
S_0	000	000	00001
S_1	001	001	00010
S_2	010	011	00100
S_3	011	010	01000
S_4	100	110	10000

Binary State Encoding

 

y_1	y_2	x	y_1	y_2	J_1	K_1	J_2	K_2	z
0	0	0	0	0	0	X	0	X	0
0	0	1	0	1	0	X	1	X	0
0	1	0	0	1	0	X	X	0	0
0	1	1	1	0	1	X	X	1	0
1	0	0	1	1	X	0	1	X	0
1	0	1	1	0	X	0	0	X	1
1	1	0	0	0	X	1	X	1	0
1	1	1	1	0	X	0	X	1	0

Simplified flip-flop input equations

		Y_1Y_2			
		x	00	01	11
0	0	0	0	0	1
	1	0	1	1	1

$$D_1 = y_1y_2' + y_2x$$

		Y_1Y_2			
		x	00	01	11
0	0	0	1	0	1
	1	1	0	0	1

$$D_2 = y_1y_2' + y_1'y_2x' + y_1'y_2'x$$

2 2-input AND, 2 3-input AND, 1 2-input OR, 1 3-input OR gates

		Y_1Y_2			
		x	00	01	11
0	0	0	0	X	X
	1	0	1	X	X

$$J_1 = x + y_2$$

		Y_1Y_2			
		x	00	01	11
0	0	X	X	0	1
	1	X	X	0	0

$$K_1 = x' + y_2'$$

		Y_1Y_2			
		x	00	01	11
0	0	0	X	X	1
	1	1	X	X	0


$$J_2 = (y_1 + x)(y_1' + x')$$

		Y_1Y_2			
		x	00	01	11
0	0	X	0	1	X
	1	X	1	1	X

$$K_2 = y_1 + x$$

4 2-input OR, 1 2-input AND gates

Gray State Encoding

 

y_1	y_2	x	y_1	y_2	J_1	K_1	J_2	K_2	z
0	0	0	0	0	0	X	0	X	0
0	0	1	0	1	0	X	1	X	0
0	1	0	0	1	0	X	X	0	0
0	1	1	1	1	1	X	X	0	0
1	0	0	0	0	X	1	0	X	0
1	0	1	1	1	X	0	1	X	0
1	1	0	1	0	X	0	X	1	0
1	1	1	1	1	X	0	X	0	1

Simplified flip-flop input equations

		Y_1Y_2			
		x	00	01	11
0	0	0	0	1	0
	1	0	1	1	1

$$D_1 = y_1y_2 + y_2x + y_1x$$

		Y_1Y_2			
		x	00	01	11
0	0		1		
	1	1	1	1	1

$$D_2 = y_1'y_2 + x$$

4 2-input AND, 1 3-input OR, 1 2-input OR gates

		Y_1Y_2			
		x	00	01	11
0	0	0	0	X	X
	1	0	1	X	X

$$J_1 = xy_2$$

		Y_1Y_2			
		x	00	01	11
0	0	X	X	0	1
	1	X	X	0	0

$$K_1 = x'y_2'$$

		Y_1Y_2			
		x	00	01	11
0	0	0	X	X	0
	1	1	X	X	1


$$J_2 = x$$

		Y_1Y_2			
		x	00	01	11
0	0	X	0	1	X
	1	X	0	0	X

$$K_2 = y_1x'$$

3 2-input AND

One-Hot State Encoding

 

y_1	y_2	y_3	y_4	x	y_1	y_2	y_3	y_4	J_1	K_1	J_2	K_2	J_3	K_3	J_4	K_4	z
0	0	0	1	0	0	0	0	1	0	X	0	X	0	X	X	0	0
0	0	0	1	1	0	0	1	0	0	X	0	X	1	X	X	1	0
0	0	1	0	0	0	0	1	0	0	X	0	X	X	0	0	X	0
0	0	1	0	1	0	1	0	0	0	X	1	X	0	1	0	X	0
0	1	0	0	0	1	0	0	0	1	X	X	1	0	X	0	X	0
0	1	0	0	1	0	1	0	0	0	X	X	0	0	X	0	X	1
1	0	0	0	0	0	0	0	1	X	1	0	X	0	X	1	X	0
1	0	0	0	1	0	1	0	0	X	1	1	X	0	X	0	X	0

Simplified flip-flop input equations

$$D_1 = y_2x'$$

$$D_2 = y_3x$$

$$D_3 = y_4x + y_3x'$$

$$D_4 = y_4x' + y_1x'$$

6 2-input AND, 2 2-input OR gates

$$J_1 = y_2x'$$

$$K_1 = 1$$

$$J_2 = y_3x + y_1x$$

$$K_2 = y_2x'$$

$$J_3 = y_4x$$

$$K_3 = y_3x$$

$$J_4 = y_1x'$$


$$K_4 = y_4x$$

5 2-input AND, 1 2-input OR gates

State Assignment

Paper & Pencil Methods

 
Alternative heuristics based on input and output behavior as well as transitions:



Highest Priority


Adjacent assignments to:

 states that share a common next state
 (group 1's in next state map)



Medium Priority

 states that share a common ancestor state
 (group 1's in next state map)




Lowest Priority

states that have common output behavior
 (group 1's in output map)

State Assignment

Pencil and Paper Methods

Example: 3-bit Sequence Detector

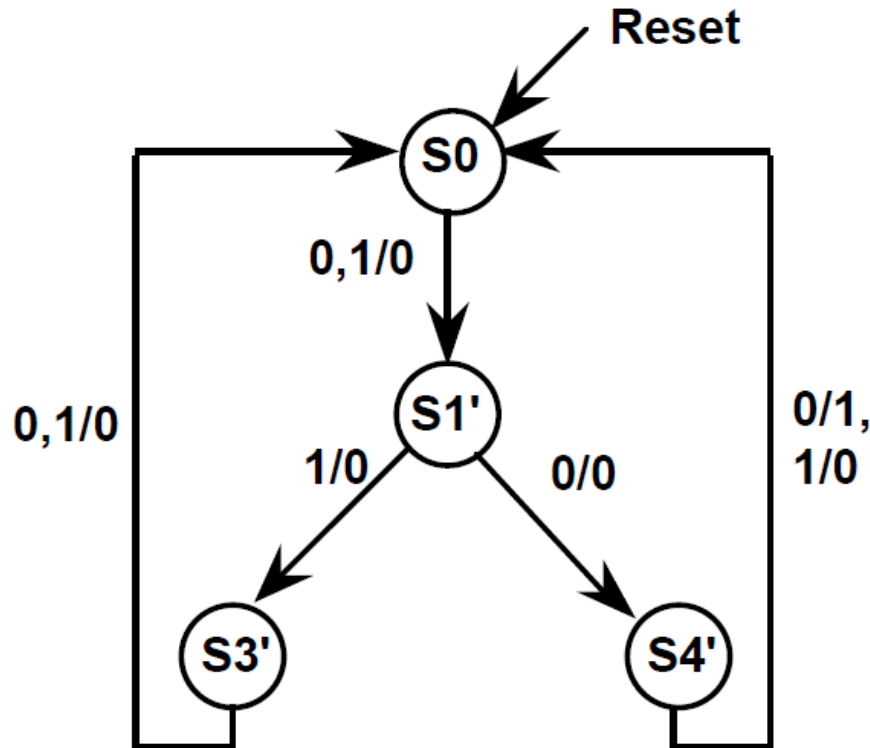

Highest Priority: (S3', S4')

Medium Priority: (S3', S4')

Lowest Priority:

0/0: (S0, S1', S3')

1/0: (S0, S1', S3', S4')

Example 1: State Assignment

- Reset State: S0
- Highest Priority: S3, S4
- Medium Priority: S3, S4
- Lowest Priority:
 - S0, S1
 - S1, S3
 - S1, S4
 - S3, S0
 - S4, S0

S0: 00

S3: 01

S4: 11

S1: 10

S0: 00

S3: 11


S4: 10

S1: 01

State Assignment

Paper & Pencil Methods

Another Example: 4 bit String Recognizer

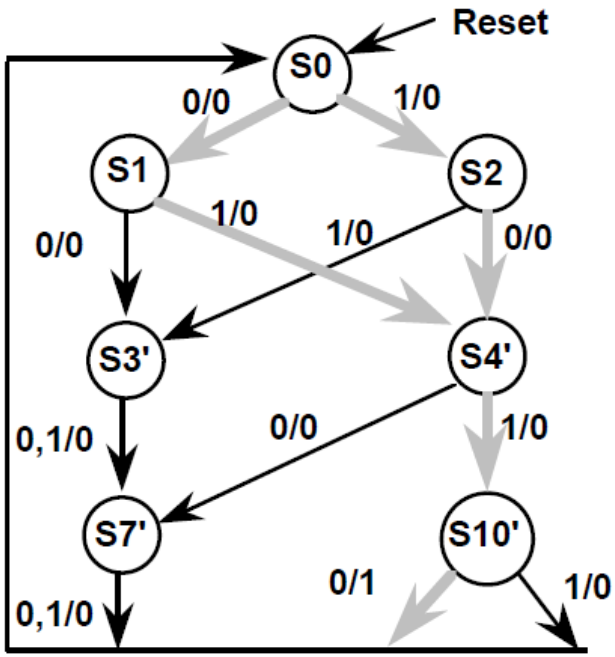

Highest Priority: (S3', S4'), (S7', S10')

Medium Priority:
(S1, S2), 2x(S3', S4'), (S7', S10')

Lowest Priority:
0/0: (S0, S1, S2, S3', S4', S7')
1/0: (S0, S1, S2, S3', S4', S7')

Example 2: State Assignment

- Reset State: S0
 - Highest Priority:
 - S1, S2
 - S3, S4
 - S7, S10
 - Medium Priority:
 - S1, S2
 - S3, S4
 - S7, S10
 - Lowest Priority:
 - S0, S1
 - S0, S2
 - S1, S3
 - S1, S4
 - S2, S3
 - S2, S4
 - S7, S0
 - S10, S0
- S0: 000
S1: 001
S2: 011
S3: 010
S4: 110
S7: 100
S10: 101

Example 2: State Assignment

y_1	y_2	y_3	x	Y_1	Y_2	Y_3	J_1	K_1	J_2	K_2	J_3	K_3	z
0	0	0	0	0	0	1	0	X	0	X	1	X	0
0	0	0	1	0	1	1	0	X	1	X	1	X	0
0	0	1	0	0	1	0	0	X	1	X	X	1	0
0	0	1	1	1	1	0	1	X	1	X	X	1	0
0	1	0	0	1	0	0	1	X	X	1	0	X	0
0	1	0	1	1	0	0	1	X	X	1	0	X	0
0	1	1	0	1	1	0	1	X	X	0	X	1	0
0	1	1	1	0	1	0	0	X	X	0	X	1	0
1	0	0	0	0	0	0	X	1	0	X	0	X	0
1	0	0	1	0	0	0	X	1	0	X	0	X	0
1	0	1	0	0	0	0	X	1	0	X	X	1	1
1	0	1	1	0	0	0	X	1	0	X	X	1	0
1	1	0	0	1	0	0	X	0	X	1	0	X	0
1	1	0	1	1	0	1	X	0	X	1	1	X	0
1	1	1	0	X	X	X	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X	X	X	X

Simplified flip-flop input equations

		Y_1Y_2			
		00	01	11	10
Y_3X	00	0	1	1	0
	01	0	1	1	0
	11	1	0	X	0
	10	0	1	X	0

$$D_1 = y_2y_3' + y_1'y_2'y_3x + y_2y_3x'$$

		Y_1Y_2			
		00	01	11	10
Y_3X	00	0	0	0	0
	01	1	0	0	0
	11	1	1	X	0
	10	1	1	X	0

$$D_2 = y_1'y_2'x + y_1'y_3$$

		Y_1Y_2			
		00	01	11	10
Y_3X	00	1	0	0	0
	01	1	0	1	0
	11	0	0	X	0
	10	0	0	X	0

$$D_2 = y_1'y_2'y_3' + y_1y_2x$$

Simplified flip-flop input equations

		y_1y_2			
		00	01	11	10
y_3x	00	0	1	X	X
	01	0	1	X	X
	11	1	0	X	X
	10	0	1	X	X

		y_1y_2			
		00	01	11	10
y_3x	00	X	X	0	1
	01	X	X	0	1
	11	X	X	X	1
	10	X	X	X	1

		$J_1 = y_2y_3' + y_2'y_3x + y_2x'$			
		00	01	11	10
y_3x	00	0	X	X	0
	01	1	X	X	0
	11	1	X	X	0
	10	1	X	X	0

		$K_1 = y_2'$			
		00	01	11	10
y_3x	00	X	1	1	X
	01	X	1	1	X
	11	X	0	X	X
	10	X	0	X	X

		$J_2 = y_1'(y_3+x)$			
		00	01	11	10
y_3x	00	1	0	0	0
	01	1	0	1	0
	11	X	X	X	X
	10	X	X	X	X

		$K_2 = y_3'$			
		00	01	11	10
y_3x	00	X	X	X	X
	01	X	X	X	X
	11	1	1	X	1
	10	1	1	X	1

$$J_3 = y_1'y_2' + y_1y_2x$$

$$K_3 = 1$$